



**ABASYN UNIVERSITY PESHAWAR**  
**DEPARTMENT OF COMPUTER SCIENCE**

## **LAB # (8)**

---

**Subject: applied physics**

**Class /section: CC**

**Submitted to: engr pasha**

**Submitted by: Hasnat Ahmad**

**Id: 21708**

**Date: 15/01/2023**

---

## EXPERIMENT NO – 09: HALF WAVE RECTIFIER

### OBJECTIVE:


- To construct a half wave rectifier and analyze its output waveform on oscilloscope.

### APPARATUS:

- Low-voltage AC power supply
- One 1N4001 diode
- Resistance  $100\Omega$
- Oscilloscope
- Transformer

The diode need not be an exact model 1N4001. Any of the "1N400X" series of rectifying diodes are suitable for the task.


### SCHEMATIC DIAGRAM:

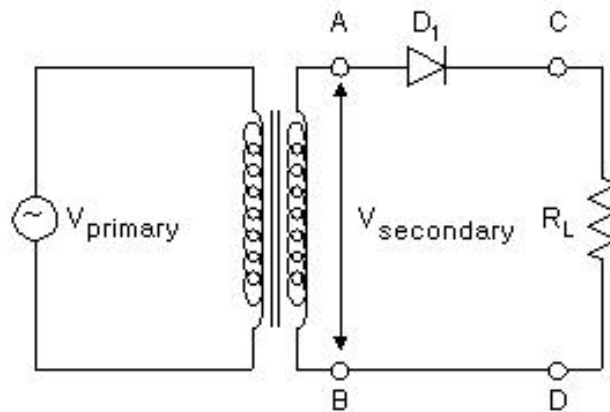

**Figure 1**


### PROCEDURE:

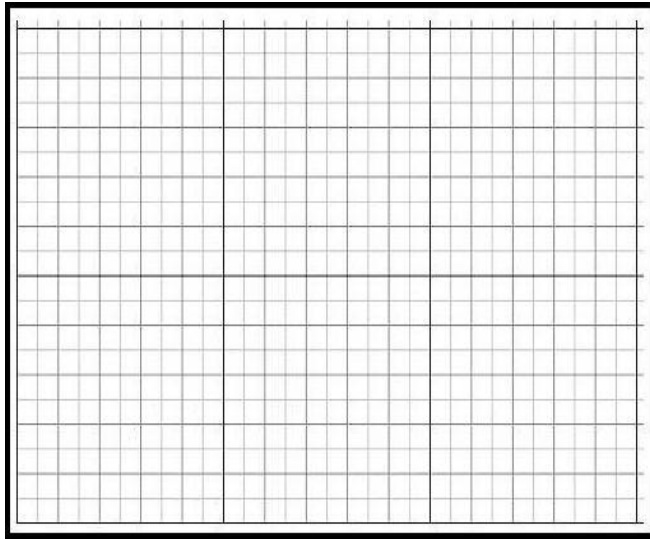1. Connect the diode to the low-voltage AC power supply as shown in a figure. Note that the resistor uses to limit the current.
2. Connect CH1 of oscilloscope to Input and CH2 to Output/Load Resistance of a circuit.
3. Switch on the oscilloscope and the sinusoidal supply.
4. Sketch the input waveform



**INPUT WAVEFORM**

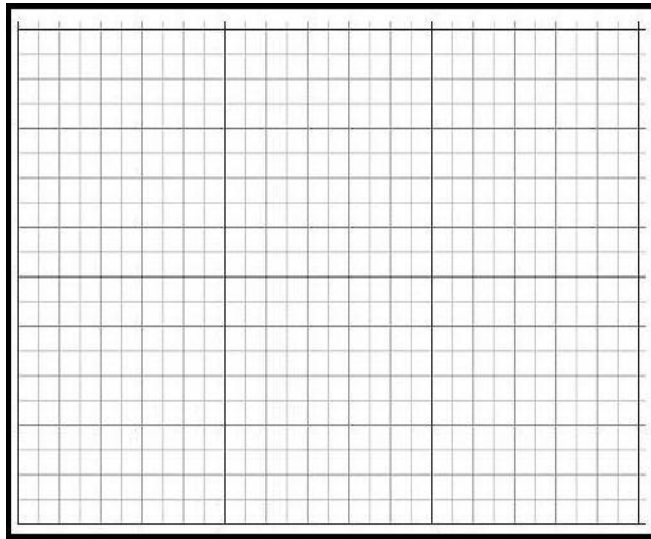6. Sketch the waveform and label it to show the periods when the diode is conducting and those when it is not.



**OUTPUT WAVEFORM**

## CONCLUSION:

forward biased diode passed current only in forward direction therefore only half wave is form in half wave rectifier.

